
32-BIT- CARRY-LOOK-ADDER

The parallel adder is a ripple carry adder type in which the carry output of each full-adder stage is connected to the carry input of the next higher-order stage. Therefore, the sum and carry outputs of any stage cannot be produced until the input carry occurs; this leads to a time delay in the addition process. This delay is known as carry propagation delay.

One method of speeding up this process by eliminating inter stage carry delay is called look ahead-carry addition.

Step-1: Implementation of 4 bit carry-look ahead adder

```
\label{eq:module adder4bit(a,b, cin, sum,cout);} \\ input [3:0] a,b; \\ input cin; \\ output [3:0] sum; \\ output cout; \\ wire [3:0] p,g,c; \\ assign p=a^b; \\ assign g=a&b; \\ assign c[0]=cin; \\ assign c[1]=g[0]|(p[0]&c[0]); \\ assign c[2]=g[1] \mid (p[1]&g[0]) \mid p[1]&p[0]&c[0]; \\ assign c[3]=g[2] \mid (p[2]&g[1]) \mid p[2]&p[1]&g[0] \mid p[2]&p[1]&p[0]&c[0]; \\ assign cout=g[3] \mid (p[3]&g[2]) \mid p[3]&p[2]&g[1] \mid p[3]&p[2]&p[1]&g[0] \mid p[3]&p[2]&p[1]&p[0]&c[0]; \\ assign sum=p^c; endmodule \\ \\ \end{aligned}
```

 

Step-2: Implementation of 32 bit carry-look ahead adder

```
Instantiate of four 4bit carry-look ahead adder to design 32 bit carry-look ahead adder. module cla32bitadder(a,b, cin, sum,cout); input [31:0] a,b;
```


input cin;

output [31:0] sum;

output cout;


wire c1,c2,c3,c4,c5,c6,c7;

cla4bitadder cla1 (.a(a[3:0]), .b(b[3:0]), .cin(cin), .sum(sum[3:0]), .cout(c1)); cla4bitadder cla2 (.a(a[7:4]), .b(b[7:4]), .cin(c1), .sum(sum[7:4]), .cout(c2)); cla4bitadder cla3(.a(a[11:8]), .b(b[11:8]), .cin(c2), .sum(sum[11:8]), .cout(c3)); cla4bitadder cla4(.a(a[15:12]), .b(b[15:12]), .cin(c3), .sum(sum[15:12]), .cout(c4)); cla4bitadder cla5 (.a(a[19:16]), .b(b[19:16]), .cin(c4), .sum(sum[19:16]), .cout(c5)); cla4bitadder cla6 (.a(a[23:20]), .b(b[23:20]), .cin(c5), .sum(sum[23:20]), .cout(c6)); cla4bitadder cla7(.a(a[27:24]), .b(b[27:24]), .cin(c6), .sum(sum[27:24]), .cout(c7)); cla4bitadder cla8(.a(a[31:28]), .b(b[31:28]), .cin(c7), .sum(sum[31:28]), .cout(cout)); endmodule

 


Step-4: Implementation of 32 bit pipe-lined carry-look ahead adder

```
module pipelined_cla32bitadder(input clk,
input rst,
input [31:0]a,
input [31:0]b,
input cin,
output reg[31:0]sum,
output reg cout
);
reg [31:0] a_r,b_r;
reg c_in;
wire [31:0] s_r;
wire c_r;
cla32bitadder uut(.a(a_r), .b(b_r), .cin(c_in), .sum(s_r), .cout(c_r));
always @ (posedge clk or posedge rst) begin
if(rst)
begin
end
else
begin
a_r<=a;
b r<=b;
c_in<=cin;</pre>
sum<=s_r;
cout<=c_r;
end
end
endmodule
```

 

Timing Summary:

 There are total 10 setup timing paths and 10 hold timing paths. For the designed shown above the clock is kept constant that is 10ns.



1. Path-1:

Source(Launch FF): b_r_reg[0]/C
Destination (Capture FF): sum_reg[30]/D

Source clock path: clock clk rise edge + net + buffer + FDCE (Prop_fdce_C) = 5.228ns

Data path: FDCE (Prop_fdce_C_Q) + net + buffer + LUT + SU = 6.786ns.

Arrival time : 5.228 + 6.786 = 12.014ns.

Required time: $\operatorname{clock} \operatorname{clk} \operatorname{rise} \operatorname{edge} + \operatorname{net} + \operatorname{buff} + \operatorname{cp} + \operatorname{cu} = 15.069 \operatorname{ns}.$

Slack = Required time - Arrival time

= 15.069 - 12.01

Destination capture delay=Required time - clock period

=15.069 - 10 = 5.069ns

= 3.055ns

2. Path-2:

Source(Launch FF): b_r_reg[0]/C
Destination (Capture FF): sum reg[29]/D

Source clock path: clock clk rise edge + net + buffer + FDCE (Prop_fdce_C) = 5.228ns

Data path: FDCE (Prop_fdce_C_Q) + net + buffer + LUT + SU = 6.699ns.

Arrival time: 5.228 + 6.786 = 11.926ns.

Required time: $\operatorname{clock} \operatorname{clk} \operatorname{rise} \operatorname{edge} + \operatorname{net} + \operatorname{buff} + \operatorname{cp} + \operatorname{cu} = 15.064 \operatorname{ns}.$

Slack = Required time - Arrival time

= 15.064 - 11.926

= 3.138ns

Destination capture delay=Required time - clock period

=15.064 - 10 = 5.064ns

3. Path-3:

Source(Launch FF): b_r_reg[0]/C
Destination (Capture FF): sum reg[25]/D

Source clock path: clock clk rise edge + net + buffer + FDCE (Prop_fdce_C) = 5.228ns

Data path: FDCE (Prop_fdce_C) = 6.031ns.

Arrival time : 5.228 + 6.031 = 11.259ns.

Required time: clock clk rise edge + net + buff + cp + cu = 14.901ns.

Slack = Required time - Arrival time = 14.901 - 11.259

Destination capture delay=Required time - clock period

=14.901 - 10 = 4.901ns

4. Path-4:

Source(Launch FF): b_r_reg[0]/C Destination (Capture FF): sum reg[28]/D

= 3.642ns

Source clock path: clock clk rise edge + net + buffer + FDCE (Prop_fdce_C) = 5.228ns Data path : FDCE (Prop_fdce_C_Q) + net + buffer + LUT + SU = 6.149ns.

Arrival time : 5.228 + 6.149 = 11.377ns.

Required time: $\operatorname{clock} \operatorname{clk} \operatorname{rise} \operatorname{edge} + \operatorname{net} + \operatorname{buff} + \operatorname{cp} + \operatorname{cu} = 15.212 \operatorname{ns}.$

Slack = Required time - Arrival time

= 15.212 - 11.377

= 3.835ns

Destination capture delay=Required time - clock period

=15.212 - 10 = 5.212ns

5. **Path-5**:

Source(Launch FF): b_r_reg[0]/C
Destination (Capture FF): sum_reg[31]/D

Source clock path: clock clk rise edge + net + buffer + FDCE (Prop_fdce_C) = 5.228ns

Data path: FDCE (Prop_fdce_C) + net + buffer + LUT + SU = 6.077ns.

Arrival time : 5.228 + 6.077 = 11.304ns.

Required time: $\operatorname{clock} \operatorname{clk} \operatorname{rise} \operatorname{edge} + \operatorname{net} + \operatorname{buff} + \operatorname{cp} + \operatorname{cu} = 15.162 \operatorname{ns}.$

Slack = Required time - Arrival time

= 15.162 - 11.304

= 3.858ns

Destination capture delay=Required time - clock period

=15.162 - 10 = 5.162ns

6. **Path-6**:

Source(Launch FF): b_r_reg[0]/C Destination (Capture FF): cout reg/D

Source clock path: clock clk rise edge + net + buffer + FDCE (Prop_fdce_C) = 5.228ns Data path : FDCE (Prop_fdce_C_Q) + net + buffer + LUT + SU = 6.073ns.

Arrival time : 5.228 + 6.073 = 11.300ns.

Required time : $\operatorname{clock} \operatorname{clk} \operatorname{rise} \operatorname{edge} + \operatorname{net} + \operatorname{buff} + \operatorname{cp} + \operatorname{cu} = 15.160 \operatorname{ns}.$

Slack = Required time - Arrival time

= 15.160 - 11.300

= 3.860ns

Destination capture delay=Required time - clock period

=15.160 - 10 = 5.160ns

7. **Path-7**:

Source(Launch FF): b_r_reg[0]/C
Destination (Capture FF): sum reg[21]/D

Source clock path: clock clk rise edge + net + buffer + FDCE (Prop_fdce_C) = 5.228ns

Data path: FDCE (Prop_fdce_C_Q) + net + buffer + LUT + SU = 6.004ns.

Arrival time : 5.228 + 6.004 = 11.232ns.

Required time: clock clk rise edge + net + buff + cp + cu = 15.210ns. **Slack** = Required time - Arrival time = 15.210 - 11.232= 3.978ns Destination capture delay=Required time - clock period =15.210 - 10= 5.210ns Source(Launch FF): b r reg[0]/C

8. **Path-8**:

Destination (Capture FF): sum reg[26]/D

Source clock path: clock clk rise edge + net + buffer + FDCE (Prop fdce C) = 5.228ns FDCE (Prop fdce C Q) + net + buffer + LUT + SU Data path: = 5.857ns.

5.228 + 5.857 = 11.084ns. Arrival time:

Required time: clock clk rise edge + net + buff + cp + cu = 15.086ns.

Slack = Required time - Arrival time

= 15.086 - 11.084

= 4.002ns

Destination capture delay=Required time - clock period

=15.086 - 10= 5.086ns

9. **Path-9**:

Source(Launch FF): b r reg[0]/C Destination (Capture FF): sum reg[22]/D

Source clock path: clock clk rise edge + net + buffer + FDCE (Prop fdce C) = 5.228ns Data path: FDCE (Prop fdce C Q) + net + buffer + LUT + SU = 5.996ns.

Arrival time: 5.228 + 5.996 = 11.224ns.

Required time: clock clk rise edge + net + buff + cp + cu = 15.251ns.

Slack = Required time - Arrival time

= 15.251 - 11.224

= 4.027ns

Destination capture delay=Required time - clock period

=15.251 - 10= 5.251ns

10. **Path-10**:

Source(Launch FF): b r reg[0]/C Destination (Capture FF): sum reg[24]/D

Source clock path: clock clk rise edge + net + buffer + FDCE (Prop fdce C) = 5.228ns Data path: FDCE (Prop fdce C Q) + net + buffer + LUT + SU = 5.887ns.

Arrival time: 5.228 + 5.887 = 11.115ns.

clock clk rise edge + net + buff + cp + cu Required time: = 15.162ns.

Slack = Required time - Arrival time

= 15.162 - 11.115

= 4.048ns

Destination capture delay=Required time - clock period

=15.162 - 10= 5.162ns

Waveform:

